

Section III simply contains the source resistor, and we have already shown in Figure 6.6 that

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{III} = \begin{bmatrix} 1 & Z_S \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 1 & 10 \\ 0 & 1 \end{bmatrix}$$

If we now cascade these transfer matrices as described by (6.2.9), we find that

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} 1 & 10 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 0 & j25 \\ j0.04 & 0 \end{bmatrix} \begin{bmatrix} 0 & j100 \\ j0.01 & 0 \end{bmatrix} \begin{bmatrix} V_L \\ Y_L V_L \end{bmatrix}$$

$$= \begin{bmatrix} -0.25 & -40 \\ 0 & -4 \end{bmatrix} \begin{bmatrix} V_L \\ Y_L V_L \end{bmatrix}$$

which means that

$$V_S = (-0.25 - 40Y_L)V_L = (-0.25 - j0.4)V_L$$

and

$$I_S = -4Y_L V_L = -j0.04V_L$$

for  $Y_L = 1/Z_L = 0.01j$ . The input impedance  $Z_{in}$  is related to  $V_S$ ,  $I_S$ , and  $Z_S$  by  $I_S = V_S/(Z_{in} + Z_S)$ , or

$$Z_{in} = \frac{V_S}{I_S} - Z_S = \frac{-0.25 - j0.4}{-j0.04} - 10 = -j6.25$$

as was also found in Example 6.1.2. The power supplied by the source is again

$$P = \frac{1}{2} \operatorname{Re}\{V_S I_S^*\} = \frac{1}{2} \operatorname{Re} \left\{ V_S \left( \frac{V_S}{10 - j6.25} \right)^* \right\}$$

$$= 0.036|V_S|^2 (\text{W})$$

### 6.3 GAMMA PLANE AND SMITH CHART ANALYSIS METHODS

Although the methods discussed in Sections 6.1 and 6.2 are adequate to solve for  $V(z)$  and  $I(z)$  everywhere on a network composed of lumped elements and TEM lines, other analysis techniques can also prove helpful. In particular, we shall consider the complex gamma plane  $\Gamma(z)$  and its mapping into complex impedance  $Z(z)$ , which is carried out graphically using a Smith chart. The Smith chart, while not so useful a computational method in this age of computers, still provides physical insight into how impedances transform on a TEM line. It is also a useful way to quickly estimate impedances that could be exactly (but more tediously!) computed analytically.

We first recall (5.3.45) and (5.3.49):

$$V(z) = V_+ e^{-jkz} + V_- e^{+jkz} \quad (6.3.1)$$

$$I(z) = Y_0 [V_+ e^{-jkz} - V_- e^{+jkz}] \quad (6.3.2)$$

These equations become

$$V(z) = V_+ e^{-jkz}[1 + \Gamma(z)] \quad (6.3.3)$$

$$I(z) = Y_0 V_+ e^{-jkz}[1 - \Gamma(z)] \quad (6.3.4)$$

where

$$\Gamma(z) \equiv \frac{V_- e^{jkz}}{V_+ e^{-jkz}} = \Gamma_L e^{2jkz} \quad (6.3.5)$$

and  $\Gamma_L = \Gamma(z=0) = V_-/V_+ = (Z_L - Z_0)/(Z_L + Z_0)$  from (6.1.4). It follows that

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \left( \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \right) \quad (6.3.6)$$

where  $\Gamma(z)$  and hence  $Z(z)$  are periodic functions of position  $z$ . Equivalently,

$$\Gamma(z) = \frac{Z_n(z) - 1}{Z_n(z) + 1} \quad (6.3.7)$$

where the *normalized impedance*  $Z_n(z)$  is defined as  $Z(z)/Z_0$ .

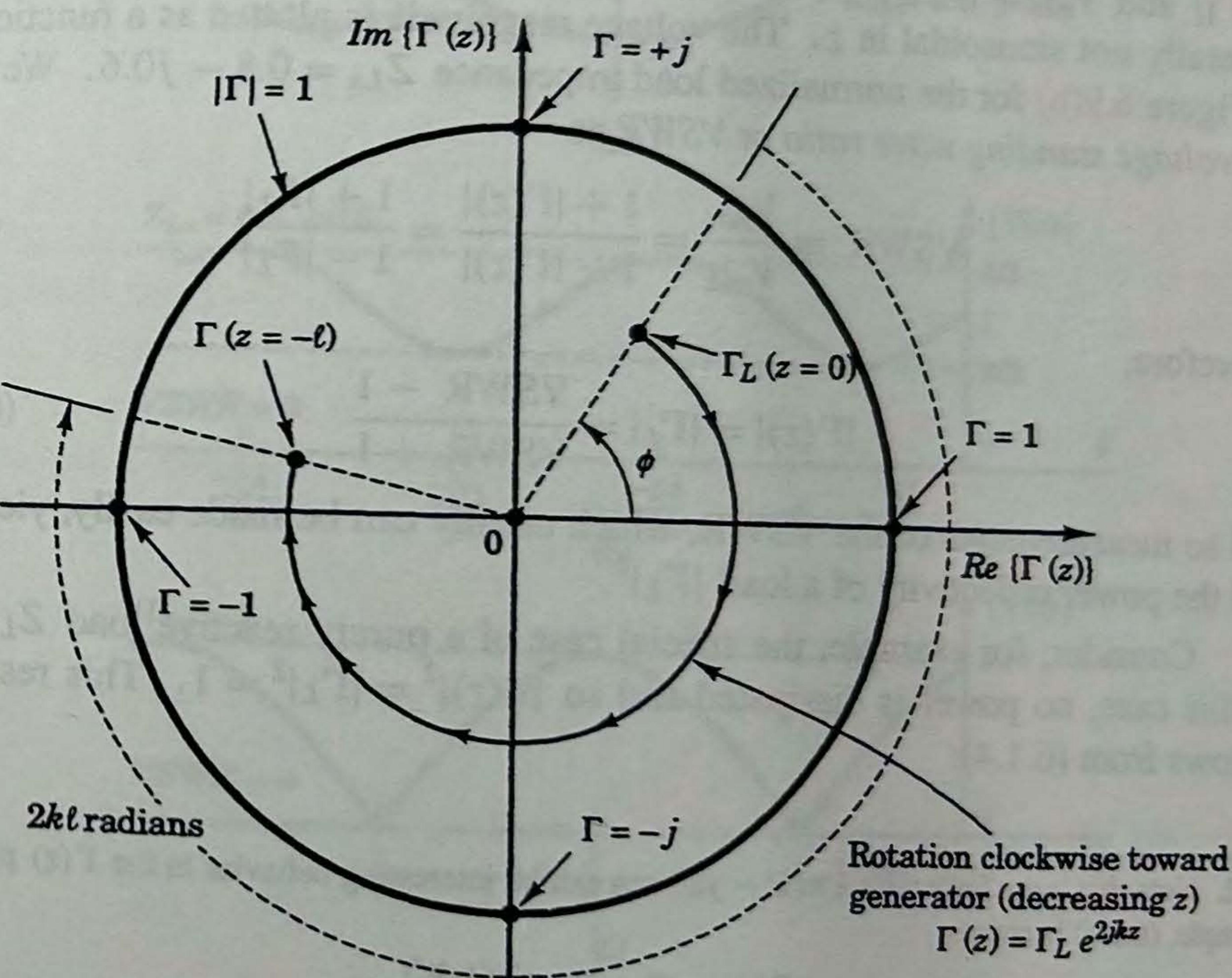


Figure 6.8 Complex gamma plane for  $\Gamma(z)$ .

Before considering the one-to-one mapping [given by (6.3.6) and (6.3.7)] between  $\Gamma(z)$  and  $Z_n(z)$  that motivated invention of the Smith chart, we first establish the character of  $\Gamma(z)$  and the relationship between  $\Gamma(z)$  and the total line voltage  $V(z)$ . The complex *gamma plane* is illustrated in Figure 6.8, having axes  $\operatorname{Re}\{\Gamma\}$  and  $\operatorname{Im}\{\Gamma\}$ . From (6.3.5), we note immediately that  $|\Gamma(z)| = |\Gamma_L|$ .<sup>1</sup> If we use (6.3.5) to plot  $\Gamma(z)$  in the gamma plane, we find that as we move in the negative

<sup>1</sup> In this analysis, we assume that the characteristic impedance  $Z_0$  is a real number so that  $k$  is also real.

$z$  direction away from the load  $Z_L$ , the angle of  $\Gamma(z)$  decreases with negative  $z$ . Therefore,  $\Gamma(z)$  rotates clockwise along a circle of radius  $|\Gamma_L|$  as  $z$  moves away from the load, one complete revolution occurring each time that  $2k\Delta z$  equals  $2\pi$ , or  $\Delta z = \lambda/2$ .

The voltage magnitude is found from (6.3.3) to be

$$|V(z)| = |V_+| |1 + \Gamma(z)| \quad (6.3.8)$$

which is represented graphically in Figure 6.9(a), where  $1 + \Gamma(z)$  is the complex vector connecting the point  $-1$  and  $\Gamma(z)$  in the gamma plane. For lossless passive media, we have already mentioned that  $|\Gamma(z)| \leq 1$ , because the reflected power must not exceed the incident power at a junction.<sup>2</sup>

This geometric construction shows how  $|V(z)|$  varies between  $V_{\max} = |V_+|(1 + |\Gamma|)$  and  $V_{\min} = |V_+|(1 - |\Gamma|)$  with a period  $\Delta z = \lambda/2$ . The pattern  $|V(z)|$  is generally not sinusoidal in  $z$ . The voltage magnitude is plotted as a function of  $z$  in Figure 6.9(b) for the normalized load impedance  $Z_{L_n} = 0.8 - j0.6$ . We define the *voltage standing wave ratio* or *VSWR* as

$$\text{VSWR} \equiv \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma(z)|}{1 - |\Gamma(z)|} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \quad (6.3.9)$$

Therefore,

$$|\Gamma(z)| = |\Gamma_L| = \frac{\text{VSWR} - 1}{\text{VSWR} + 1} \quad (6.3.10)$$

and so measurements of the VSWR, which usually can be made easily, yield  $|\Gamma_L|$  and the power reflectivity of a load  $|\Gamma_L|^2$ .

Consider, for example, the special case of a purely reactive load  $Z_L = jX$ . In this case, no power is dissipated and so  $|\Gamma(z)|^2 = |\Gamma_L|^2 = 1$ . This result also follows from (6.1.4):

2. Note that lossy lines with  $k = k' - jk''$  can exhibit interesting behavior in the  $\Gamma(z)$  plane. For example, (6.3.5) becomes

$$\Gamma(z = -\ell) = \Gamma_L e^{-2jk'\ell - 2k''\ell}$$

and  $\Gamma(z = -\ell)$  spirals exponentially inward toward  $\Gamma = 0$  as  $\ell \rightarrow \infty$ . Thus the impedance at  $z = -\ell$  approaches  $Z_0$  as  $\ell \rightarrow \infty$ . It is also interesting to note that  $|\Gamma|$  can exceed unity for a lossy line because  $Z_0 = \sqrt{(R + j\omega L)/(G + j\omega C)}$  is in general complex, and  $Z_0$  can have phase angle  $\phi$  where  $-\pi/4 < \phi < \pi/4$ . Thus,  $Z_n = Z_L/Z_0$  can have an angle  $\alpha = \beta - \phi$  up to  $\pm 3\pi/4$ . The angle  $\beta$  of  $Z_L$  is limited to  $-\pi/2 \leq \beta \leq \pi/2$  since the real part of  $Z_L$  is always positive for passive media. It can easily be seen that

$$|\Gamma| = \frac{|Z_n - 1|}{|Z_n + 1|} = \frac{||Z_n| e^{j\alpha} - 1|}{||Z_n| e^{j\alpha} + 1|}$$

is largest when  $\alpha = \pm 3\pi/4$  and  $\text{Re}\{Z_n e^{j\alpha}\}$  is negative. The maximum possible value of  $|\Gamma|$  is  $1 + \sqrt{2}$ . Note that when  $|\Gamma| > 1$  on a lossy line, it does not mean that there is power amplification. Here,  $|\Gamma| > 1$  is the result of the reactive elements, and power in the forward or reverse directions is no longer simply equal to  $|V_+|^2/2Z_0$  or  $|V_-|^2/2Z_0$  because  $Z_0$  is complex.

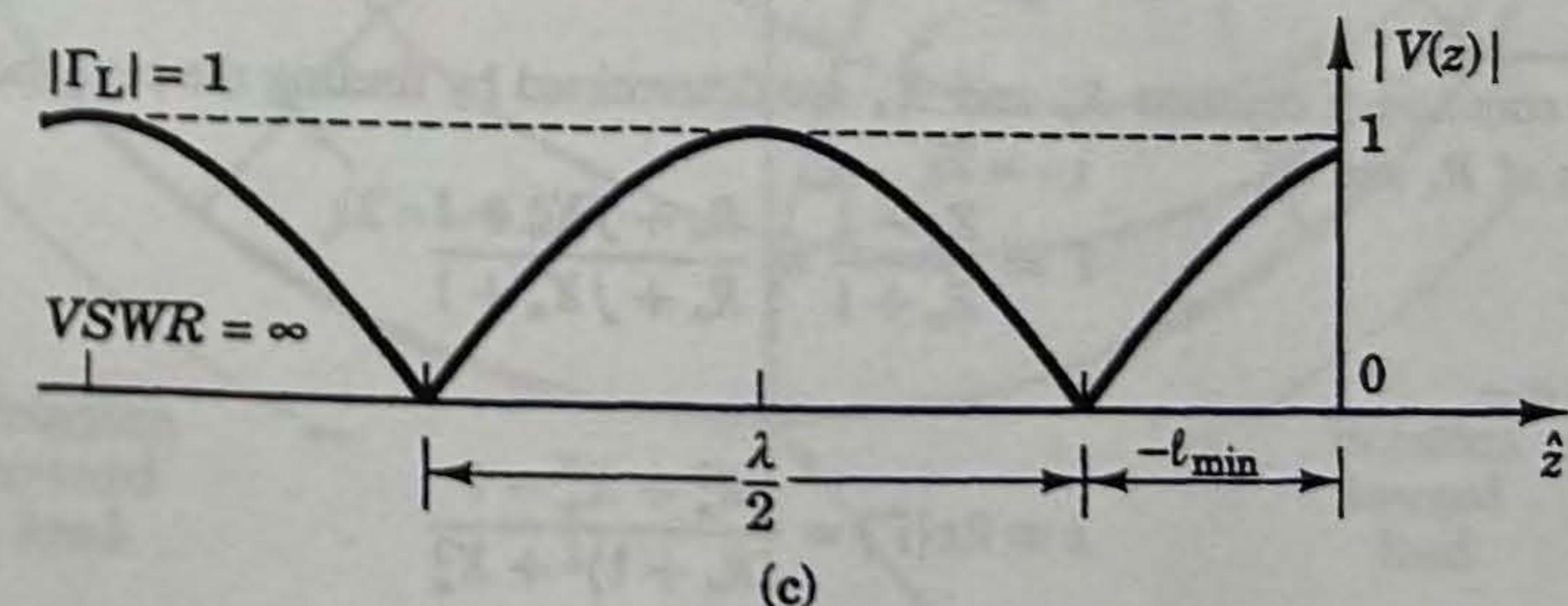
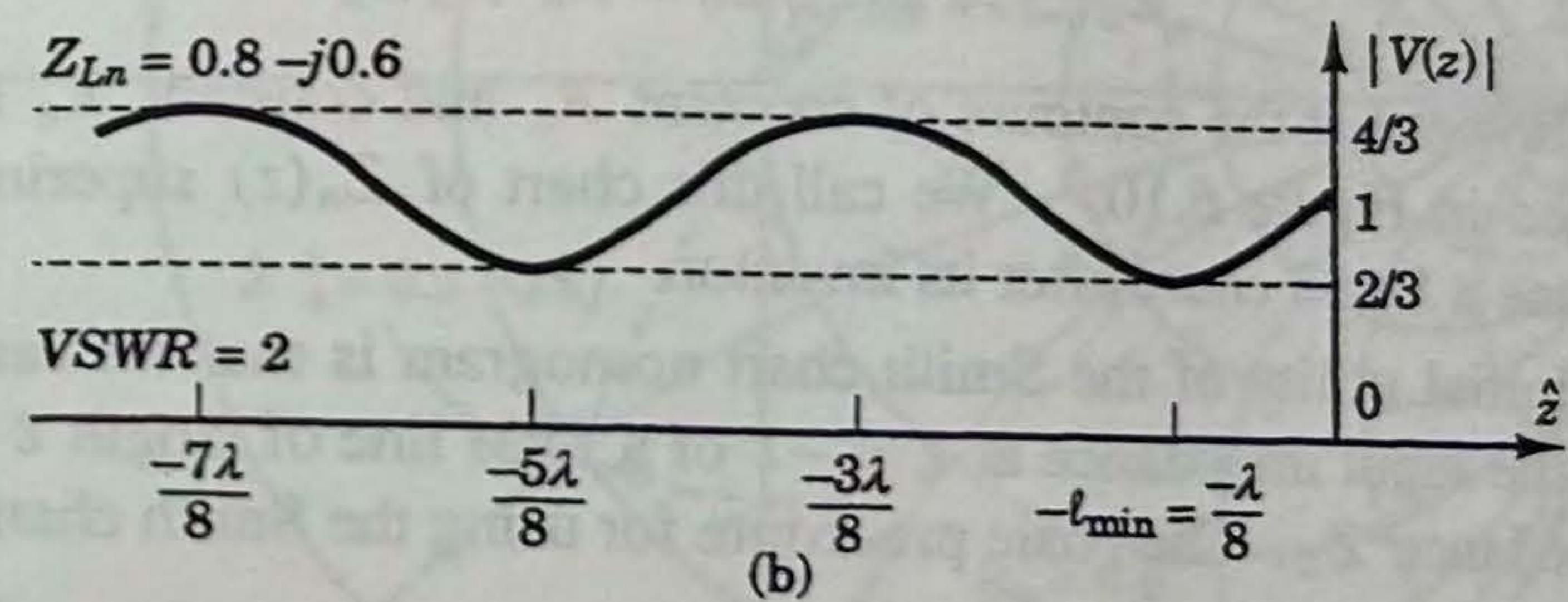
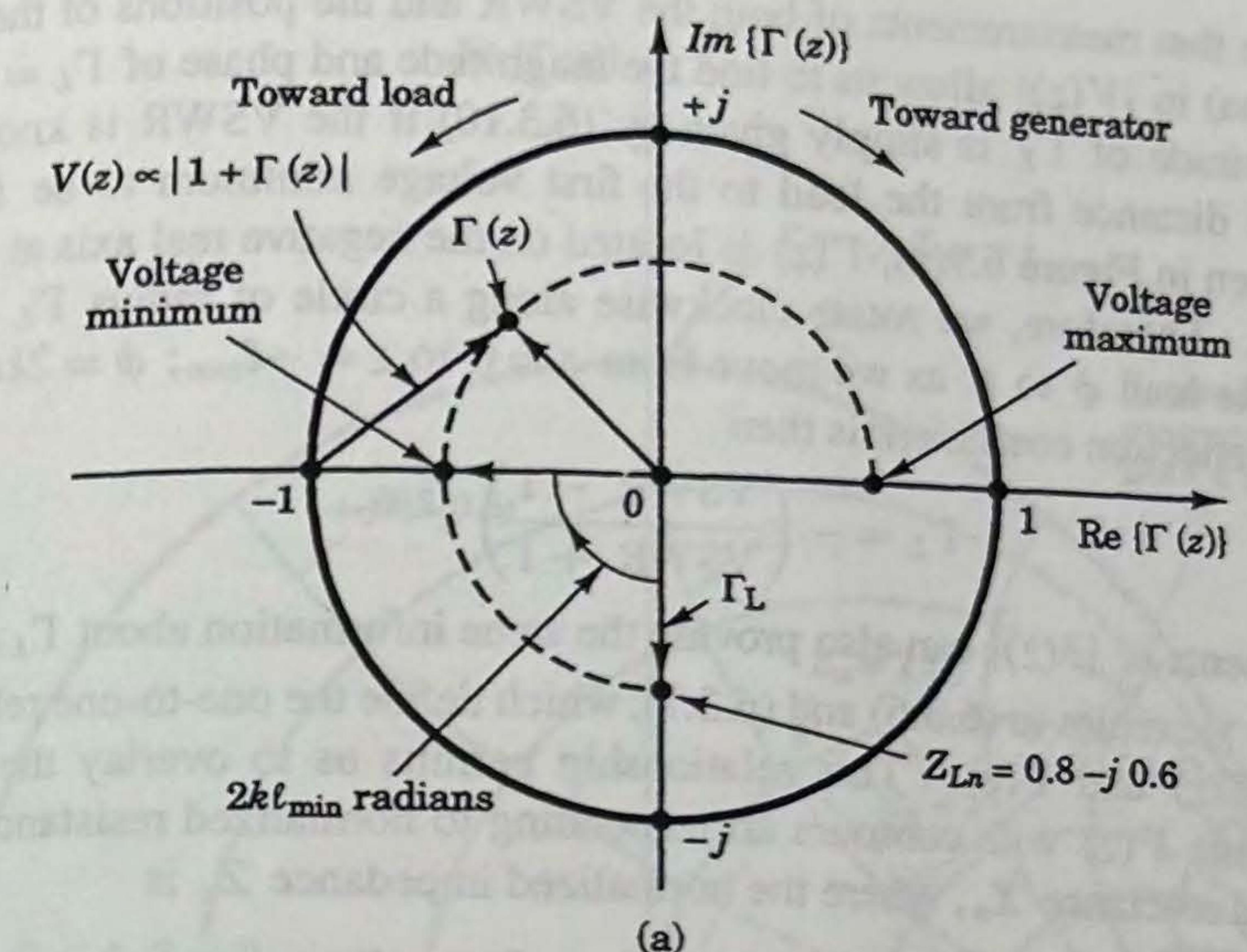


Figure 6.9 Voltage magnitude represented in the gamma plane.

$$|\Gamma_L| = \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right| = \left| \frac{jX - Z_0}{jX + Z_0} \right| = 1$$

For a purely reactive load, the VSWR defined by (6.3.9) is infinite, and  $|V(z)|$  is illustrated in Figure 6.9(c). We can also calculate  $|V(z)|$  analytically in this special case by noting that  $\Gamma_L = e^{j\phi}$  where  $\phi$  is determined from  $X$  and  $Z_0$ :  $\phi = \tan^{-1}[2XZ_0/(X^2 - Z_0^2)]$ . Equation (6.3.8) then yields

$$\begin{aligned} |V(z)| &= |V_+| |1 + e^{j\phi} e^{2jkz}| \\ &= 2|V_+| |\cos(kz - \phi/2)| \end{aligned}$$

which is exactly what is shown in Figure 6.9(c).

Note that measurements of both the VSWR and the positions of the minima (or maxima) in  $|V(z)|$  allow us to find the magnitude and phase of  $\Gamma_L = |\Gamma_L| e^{j\phi}$ . The magnitude of  $\Gamma_L$  is simply given by (6.3.10) if the VSWR is known. We define the distance from the load to the first voltage minimum to be  $\ell_{\min}$ . As may be seen in Figure 6.9(a),  $\Gamma(z)$  is located on the negative real axis at a voltage minimum. Therefore, we rotate clockwise along a circle of radius  $\Gamma_L$  from the angle of the load  $\phi$  to  $\pi$  as we move from  $z = 0$  to  $z = -\ell_{\min}$ ;  $\phi = 2k\ell_{\min} - \pi$ . The load reflection coefficient is then

$$\Gamma_L = -\left(\frac{\text{VSWR} - 1}{\text{VSWR} + 1}\right) e^{2jk\ell_{\min}} \quad (6.3.11)$$

Measurements of  $|I(z)|$  can also provide the same information about  $\Gamma_L$ .

Now we return to (6.3.6) and (6.3.7), which define the one-to-one relationship between  $Z(z)$  and  $\Gamma(z)$ . This relationship permits us to overlay the complex gamma plane  $\Gamma(z)$  with contours corresponding to normalized resistance  $R_n$  and normalized reactance  $X_n$ , where the normalized impedance  $Z_n$  is

$$Z_n(z) = Z(z)/Z_0 = R_n + jX_n$$

It can be shown that the contours of constant  $R_n$  and constant  $X_n$  are all circles, as illustrated in Figure 6.10.<sup>3</sup> We call this chart of  $Z_n(z)$  superimposed on the gamma plane a *Smith chart* after its inventor.

The initial utility of the Smith chart nomogram is that we can immediately determine the input impedance at  $z = -\ell$  of a TEM line of length  $\ell$  terminated by a load impedance  $Z_L$ . The basic procedure for using the Smith chart is as follows:

3. These contours of constant  $R_n$  and  $X_n$  are determined by finding the real and imaginary parts of  $\Gamma$  in terms of  $R_n$  and  $X_n$

$$\Gamma = \frac{Z_n - 1}{Z_n + 1} = \frac{R_n + jX_n - 1}{R_n + jX_n + 1}$$

which means that

$$x \equiv \text{Re}\{\Gamma\} = \frac{R_n^2 + X_n^2 - 1}{(R_n + 1)^2 + X_n^2}$$

and

$$y \equiv \text{Im}\{\Gamma\} = \frac{-2X_n}{(R_n + 1)^2 + X_n^2}$$

If these two equations are solved for  $x$  and  $y$  as a function of  $R_n$  alone, then after some algebra we find that

$$\left(x - \frac{R_n}{R_n + 1}\right)^2 + y^2 = \left(\frac{1}{R_n + 1}\right)^2$$

which is the equation for a circle centered at  $(R_n/(R_n + 1), 0)$  of radius  $1/(R_n + 1)$ . We note that this circle always intersects the point  $(1, 0)$  in the gamma plane. These are the contours of constant  $R_n$ .

Conversely, we may solve for  $x$  and  $y$  in terms of  $X_n$  alone, giving

$$(x - 1)^2 + \left(y + \frac{1}{X_n}\right)^2 = \left(\frac{1}{X_n}\right)^2$$

which is also the equation of a circle centered at  $(1, -1/X_n)$  with radius  $1/X_n$ . The portions of these

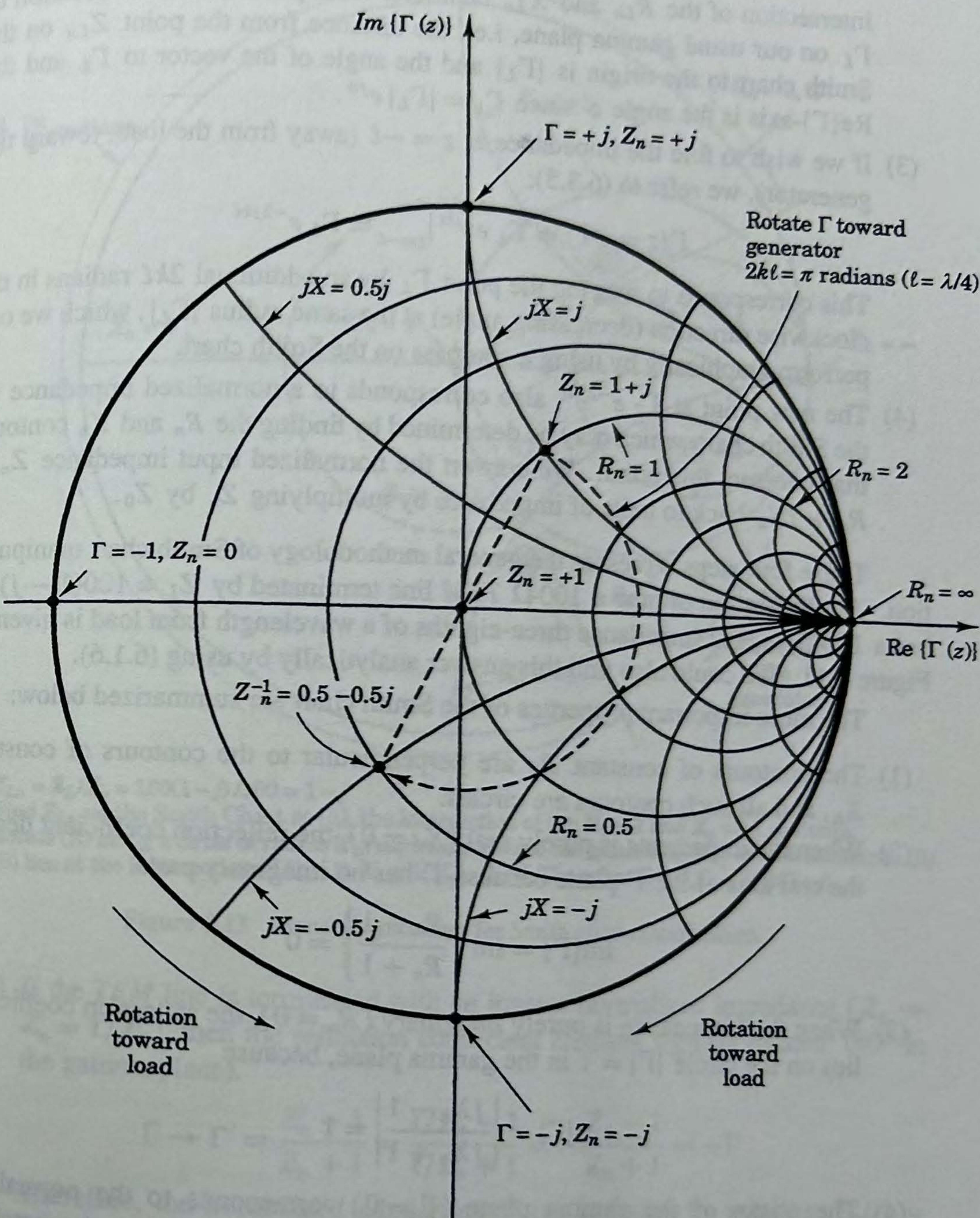


Figure 6.10 Smith chart.

- (1) Calculate the normalized load impedance by dividing  $Z_L$  by the characteristic impedance of the transmission line:  $Z_{L_n} = Z_L/Z_0$ .
- (2) Find the point  $Z_{L_n} = R_{L_n} + jX_{L_n}$  on the Smith chart by looking for the

<sup>3</sup> Circles that lie within the unit circle on the gamma plane ( $|\Gamma| < 1$ ) are the contours of constant  $X_n$ , and these circles also intersect the point  $(1, 0)$  in the  $\Gamma$ -plane.

intersection of the  $R_{L_n}$  and  $X_{L_n}$  contours. This point is also the location of  $\Gamma_L$  on our usual gamma plane, i.e., the distance from the point  $Z_{L_n}$  on the Smith chart to the origin is  $|\Gamma_L|$  and the angle of the vector to  $\Gamma_L$  and the  $\text{Re}\{\Gamma\}$ -axis is the angle  $\phi$  since  $\Gamma_L = |\Gamma_L| e^{j\phi}$ .

- (3) If we wish to find the impedance at  $z = -\ell$  (away from the load, toward the generator), we refer to (6.3.5):

$$\Gamma(z = -\ell) = \Gamma_L e^{2jkz} \Big|_{z=-\ell} = \Gamma_L e^{-2jk\ell}$$

This corresponds to rotating the point  $\Gamma_L$  by an additional  $2k\ell$  radians in the clockwise direction (decreasing angle) at the same radius  $|\Gamma_L|$ , which we can perform graphically by using a compass on the Smith chart.

- (4) The new point at  $\Gamma_L e^{-2jk\ell}$  also corresponds to a normalized impedance on the Smith chart, which may be determined by finding the  $R_n$  and  $X_n$  contours that intersect this point. We convert the normalized input impedance  $Z_n = R_n + jX_n$  back to units of impedance by multiplying  $Z_n$  by  $Z_0$ .

These four steps represent the general methodology of Smith chart manipulation. An illustration of how a  $100\Omega$  TEM line terminated by  $Z_L = 100(1-j)\Omega$  has a  $100(2+j)\Omega$  impedance three-eighths of a wavelength from load is given in Figure 6.11. We could also find this answer analytically by using (6.1.6).

The more important properties of the Smith chart are summarized below:

- (1) The contours of constant  $R_n$  are perpendicular to the contours of constant  $X_n$ , and all such contours are circles.
- (2) When the impedance is purely real ( $X_n = 0$ ), the reflection coefficient lies on the real axis of the  $\Gamma$ -plane because  $\Gamma$  has no imaginary part:


$$\text{Im}\{\Gamma\} = \text{Im} \left\{ \frac{R_n - 1}{R_n + 1} \right\} = 0$$

- (3) When the impedance is purely imaginary ( $R_n = 0$ ), the reflection coefficient lies on the circle  $|\Gamma| = 1$  in the gamma plane, because

$$|\Gamma| = \left| \frac{jX_n - 1}{jX_n + 1} \right| = 1$$

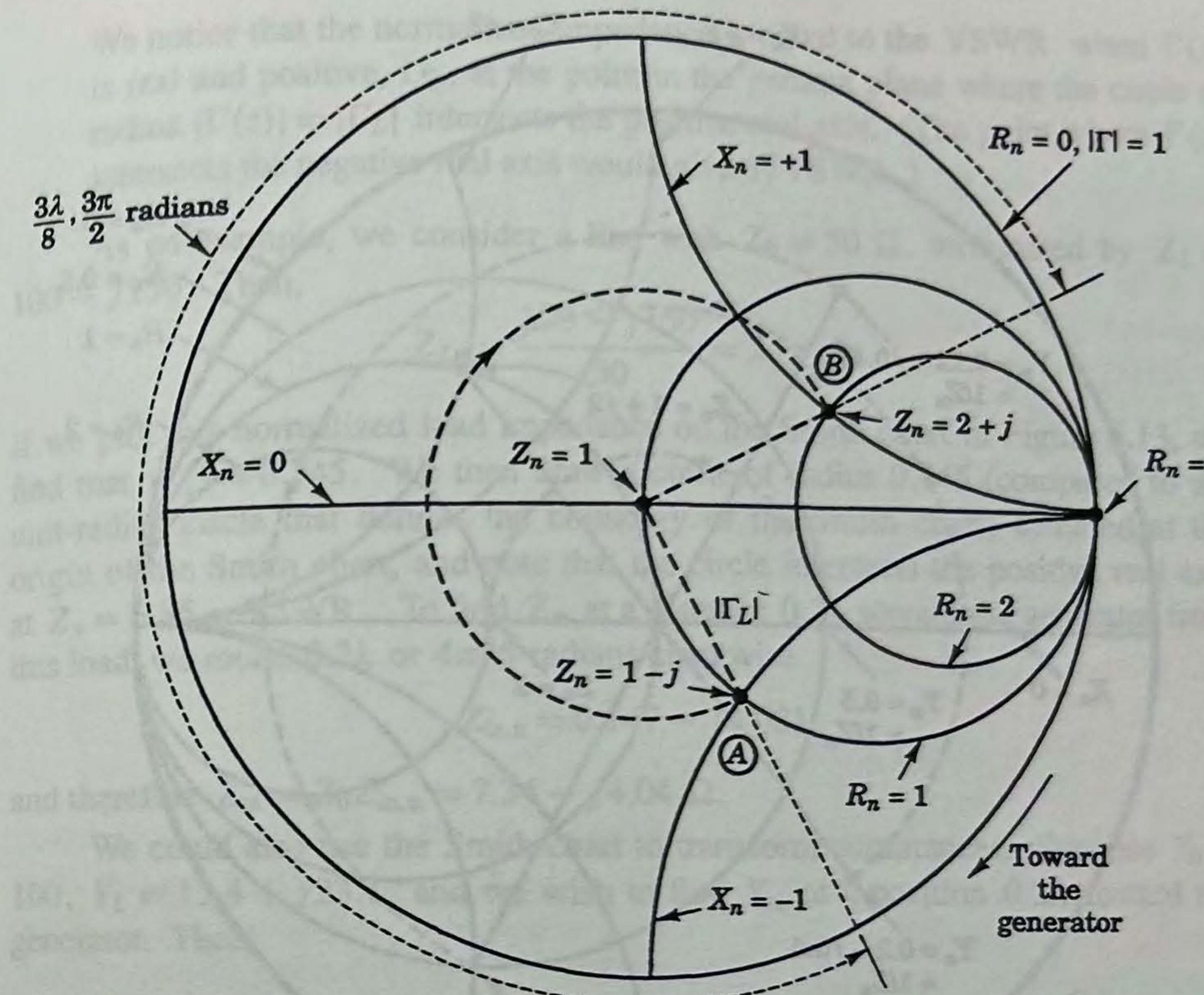- (4) The origin of the gamma plane ( $\Gamma = 0$ ) corresponds to the normalized impedance  $Z_n = 1$ , which is  $Z_0$  in un-normalized form. This is the matched-load impedance case, where no reflections are observed.
- (5) If a lossless line is terminated with the conjugate impedance  $Z_L^*$ , then the reflection coefficient must be complex conjugated also:

$$\Gamma^* = \frac{Z_n^* - 1}{Z_n^* + 1}$$



- (1)  $Z_{L_n} = Z_L/Z_0 = 100(1-j)/100 = 1-j$
- (2) Find  $Z_{L_n}$  on the Smith Chart at (A), the intersection of the  $R_n = 1$  and  $X_n = -1$  contours,
- (3) Rotate (A) along a circle of radius  $|\Gamma_L|$  clockwise toward the generator  $3\lambda/8$  or  $3\pi/2$  radians to (B).
- (4) (B) lies at the intersection of  $R_n = 2$ ,  $X_n = 1$ ;  $Z_n = 2 + j$ . Therefore  $Z = Z_n Z_0 = 100(2+j)$ .

Figure 6.11 General procedure for Smith chart manipulation.

- (6) If the TEM line is terminated with an inverse normalized impedance ( $Z_n \rightarrow Z'_n = 1/Z_n$ ), then the reflection coefficient changes sign (is rotated  $180^\circ$  in the gamma plane).

$$\Gamma \rightarrow \Gamma' = \frac{Z'_n - 1}{Z_n + 1} = \frac{1/Z_n - 1}{1/Z_n + 1} = -\frac{Z_n - 1}{Z_n + 1} = -\Gamma$$

Therefore, the normalized admittance  $Y_n(z)$  is found by rotating  $Z_n(z) = 1/Y_n(z)$  by  $180^\circ$  on the Smith chart, as illustrated for three specific cases in Figure 6.12. The Smith chart can thus be used equally well to represent impedances or admittances.

- (7) A change  $\Delta z$  in position along the transmission line is represented by rotating  $\Gamma$  by an angle  $2k\Delta z$  radians;  $\Gamma_L$  at  $z = 0$  is transformed into  $\Gamma(z)$  at position  $z$  by

$$\Gamma(z) = \Gamma_L e^{2jkz}$$

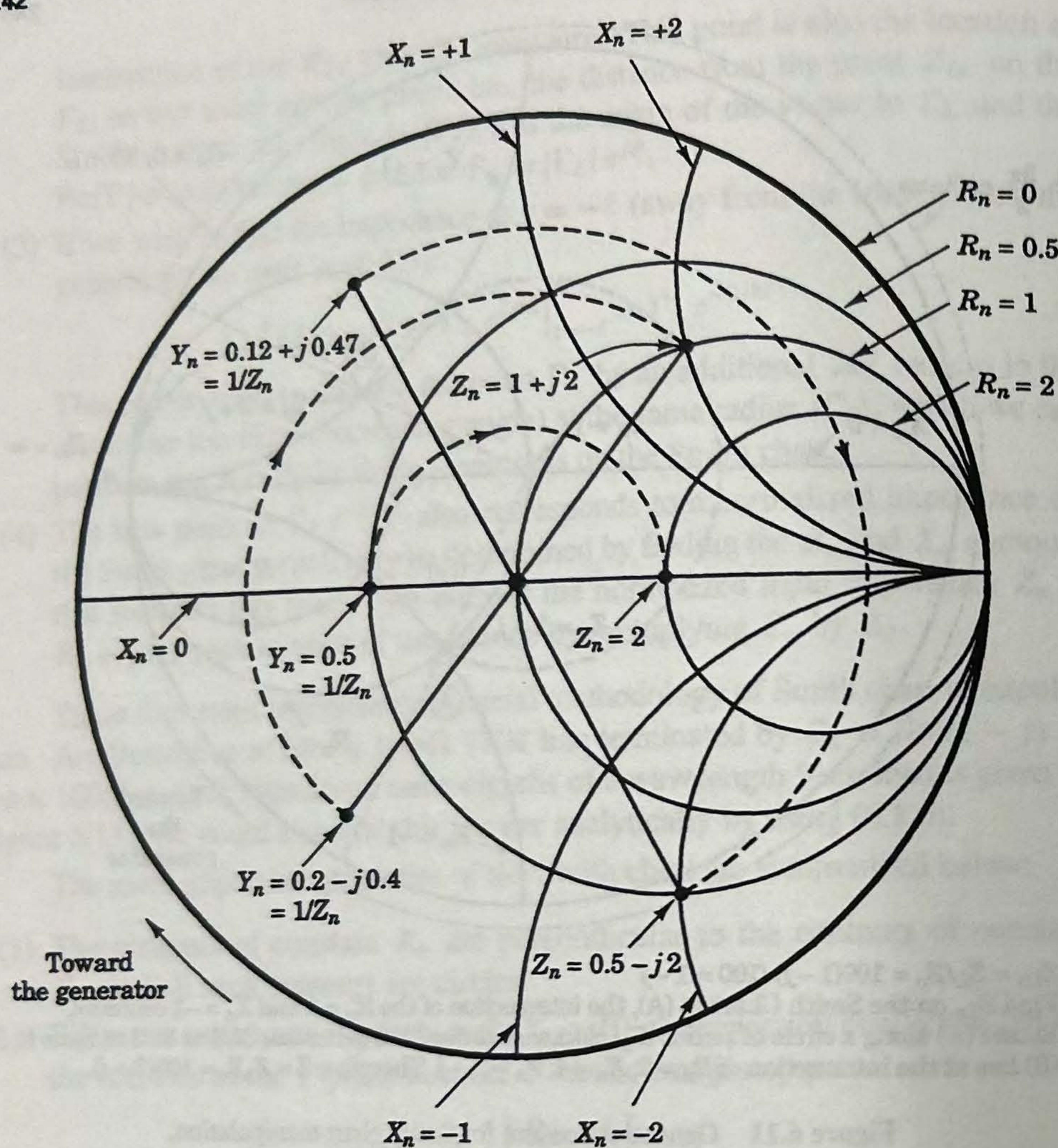


Figure 6.12 Admittances on a Smith chart.

That is, we draw a circle of radius  $|\Gamma_L|$  and rotate clockwise from  $\Gamma_L$  to determine the impedance at positions closer to the generator, and counterclockwise to determine the impedance at positions closer to the load, where the load is in the direction of increasing  $z$ . As noted earlier, a complete rotation occurs when  $2k\Delta z = 2\pi$ , or when  $\Delta z = \lambda/2$ .

- (8) The VSWR may be obtained directly from the Smith chart by comparing it with the definition of normalized impedance (6.3.9):

$$\text{VSWR} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

versus

$$Z_n(z) = \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

We notice that the normalized impedance is equal to the VSWR when  $\Gamma(z)$  is real and positive, i.e., at the point in the gamma plane where the circle of radius  $|\Gamma(z)| = |\Gamma_L|$  intersects the positive real axis. (The point where  $\Gamma(z)$  intersects the negative real axis would give  $1/\text{VSWR}$ .)

As an example, we consider a line with  $Z_0 = 50 \Omega$ , terminated by  $Z_L = 100 - j150$ . Then,

$$Z_{Ln} = \frac{100 - j150}{50} = 2 - j3$$

If we plot this normalized load impedance on the Smith chart in Figure 6.13, we find that  $|\Gamma_L| = 0.745$ . We then draw a circle of radius 0.745 (compared to the unit-radius circle that defines the boundary of the Smith chart) centered at the origin of the Smith chart, and note that the circle intersects the positive real axis at  $Z_n = 6.85 = \text{VSWR}$ . To find  $Z_{in}$  at a distance  $0.2\lambda$  toward the generator from this load, we rotate  $0.2\lambda$  or  $4\pi/5$  radians clockwise

$$Z_{in,n} = 0.147 - j0.081$$

and therefore  $Z_{in} = Z_0 Z_{in,n} = 7.34 - j4.04 \Omega$ .

We could also use the Smith chart to transform admittances. Suppose  $Y_0 = 100$ ,  $Y_L = 15.4 + j23.1$ , and we wish to find  $Y_{in}$  at a position  $0.2\lambda$  toward the generator. Then,

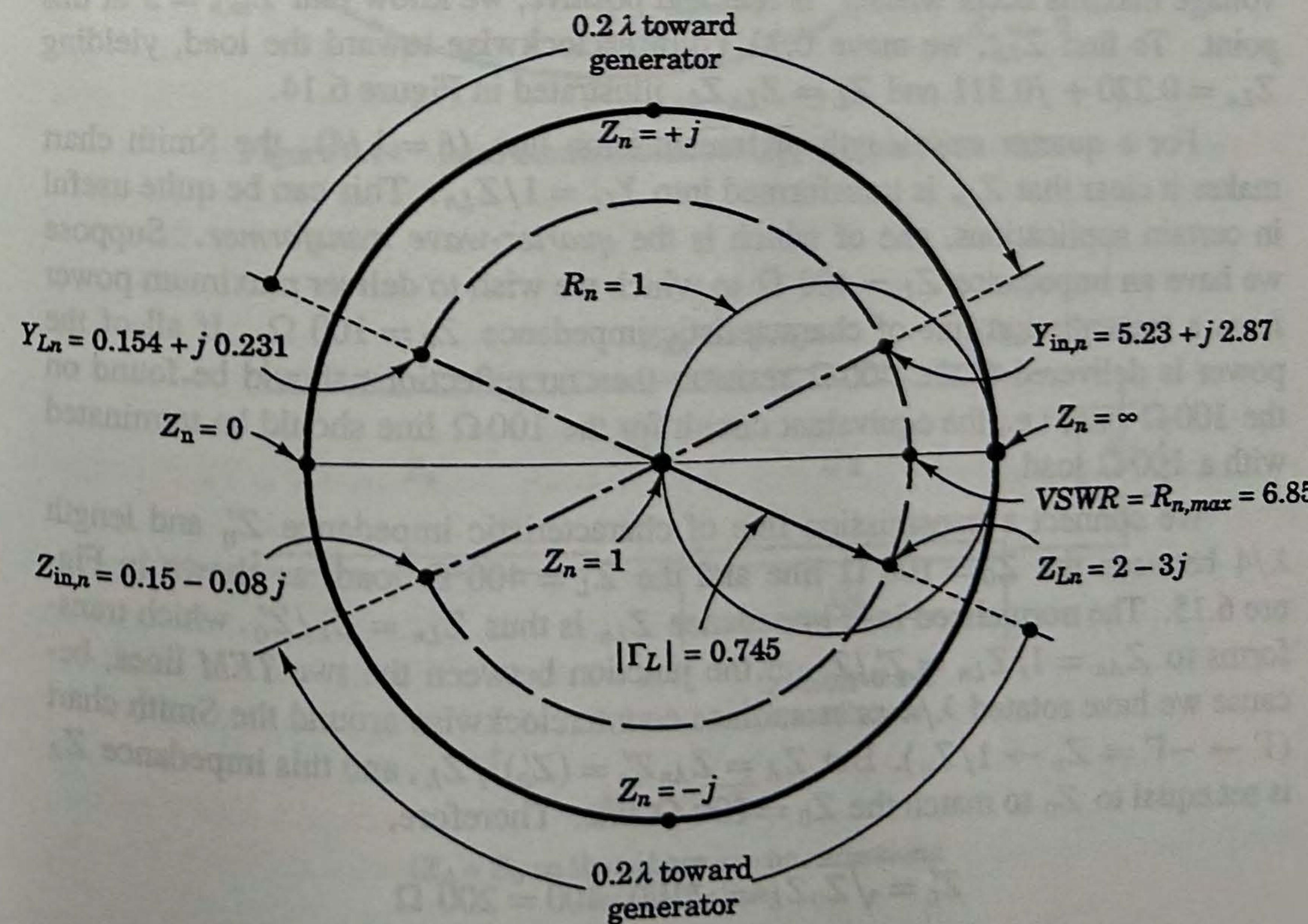


Figure 6.13 Impedance and admittance transformations using a Smith chart.

$$Y_{Ln} = Y_L / Y_0 = 0.154 + j0.231$$

which is plotted in Figure 6.13. The corresponding  $Z_{Ln}$  is directly opposite on the chart, as discussed in observation (6), and is given by  $Z_{Ln} = 2 - j3$ . We rotate this  $0.2\lambda$  clockwise to find  $Z_{in,n} = 0.147 - j0.081$  as before. The normalized admittance is then directly opposite  $Z_{in,n}$ , and is equal to  $Y_{in,n} = 5.23 + j2.87$ . The total input admittance is thus

$$Y_{in} = (5.23 + j2.87)100 = 523 + j287 \Omega^{-1}$$

But we could have also utilized admittances directly:

- (1)  $Y_{Ln} = Y_L / Y_0 = (15.4 + j23.1)/100 = 0.154 + j0.231$
- (2) Rotate  $Y_{Ln}$  clockwise (toward the generator)  $0.2\lambda$  to get  $Y_{in,n} = 5.23 + j2.87$ .
- (3)  $Y_{in} = Y_{in,n} Y_0 = 523 + j287$ .

The Smith chart can also facilitate finding  $Z_L$  from VSWR measurements. Suppose we measure the voltage maximum to be  $\ell_{max} = 0.2\lambda$  from the unknown load  $Z_L$ , and the VSWR is 5. Then we know that  $Z_{Ln}$  must lie on the  $\Gamma$  circle intercepting the point  $R_n = 5$ ,  $jX_n = 0$ , where  $\Gamma$  is real and positive. Since voltage maxima occur when  $\Gamma$  is real and positive, we know that  $Z_{in,n} = 5$  at this point. To find  $Z_{Ln}$ , we move  $0.2\lambda$  counterclockwise toward the load, yielding  $Z_{Ln} = 0.220 + j0.311$  and  $Z_L = Z_{Ln}Z_0$ , illustrated in Figure 6.14.

For a quarter wavelength of transmission line ( $\ell = \lambda/4$ ), the Smith chart makes it clear that  $Z_{Ln}$  is transformed into  $Y_{Ln} = 1/Z_{Ln}$ . This can be quite useful in certain applications, one of which is the *quarter-wave transformer*. Suppose we have an impedance  $Z_L = 400 \Omega$  to which we wish to deliver maximum power from a transmission line of characteristic impedance  $Z_0 = 100 \Omega$ . If all of the power is delivered to the  $400\Omega$  resistor, then no reflections should be found on the  $100\Omega$  line; i.e., the equivalent circuit for the  $100\Omega$  line should be terminated with a  $100\Omega$  load.

We connect a transmission line of characteristic impedance  $Z'_0$  and length  $\lambda/4$  between the  $Z_0 = 100 \Omega$  line and the  $Z_L = 400 \Omega$  load, as shown in Figure 6.15. The normalized load impedance  $Z_{Ln}$  is thus  $Z_{Ln} = Z_L / Z'_0$ , which transforms to  $Z_{An} = 1/Z_{Ln} = Z'_0 / Z_L$  at the junction between the two TEM lines, because we have rotated  $\lambda/4$  or  $\pi$  radians counterclockwise around the Smith chart ( $\Gamma \rightarrow -\Gamma \Rightarrow Z_n \rightarrow 1/Z_n$ ). But  $Z_A = Z_{An}Z'_0 = (Z'_0)^2 / Z_L$ , and this impedance  $Z_A$  is set equal to  $Z_0$  to match the  $Z_0 = 100 \Omega$  line. Therefore,

$$Z'_0 = \sqrt{Z_0 Z_L} = \sqrt{100 \cdot 400} = 200 \Omega$$

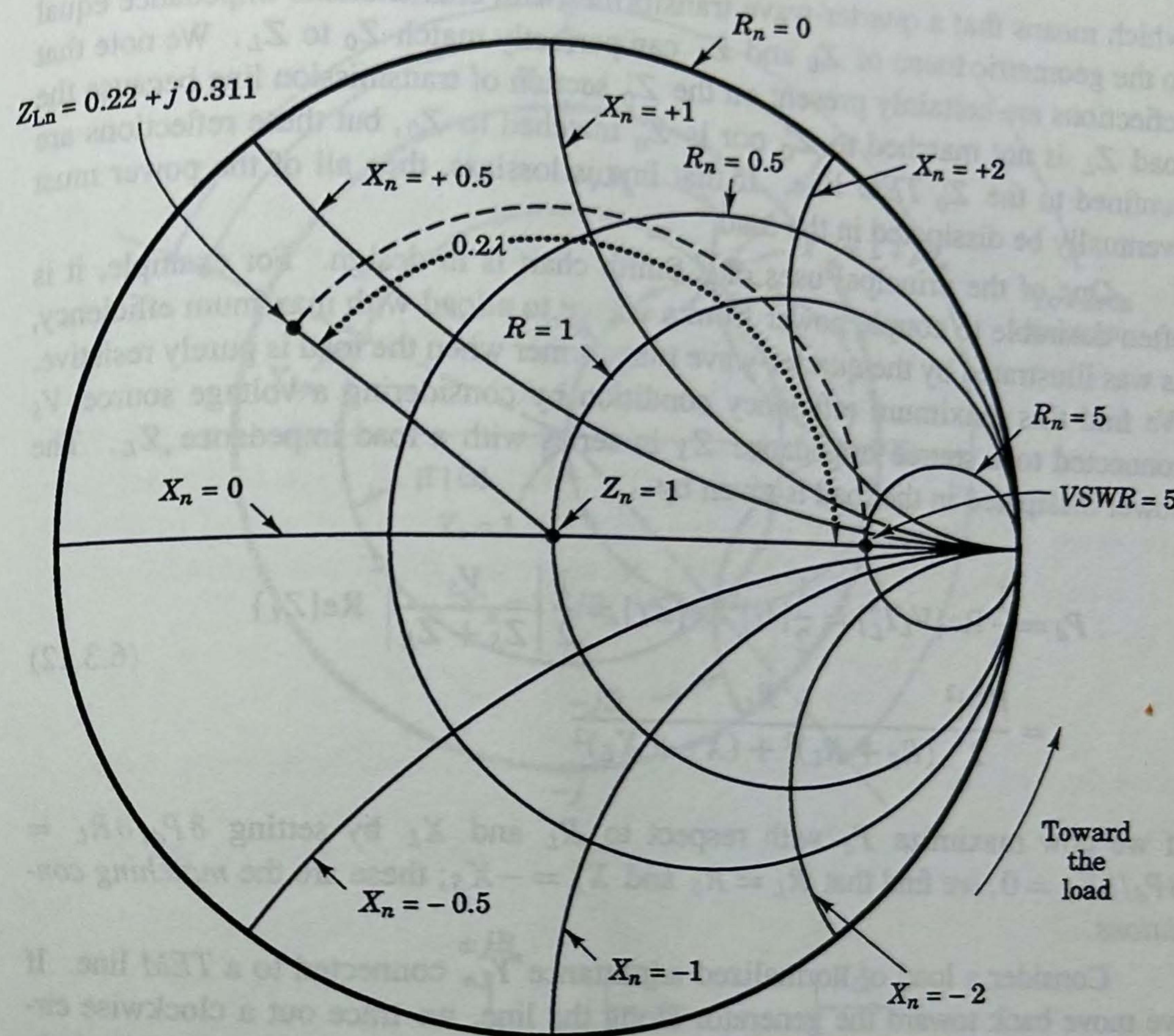


Figure 6.14 Load determination for  $Z_{Ln}$  using a Smith chart.

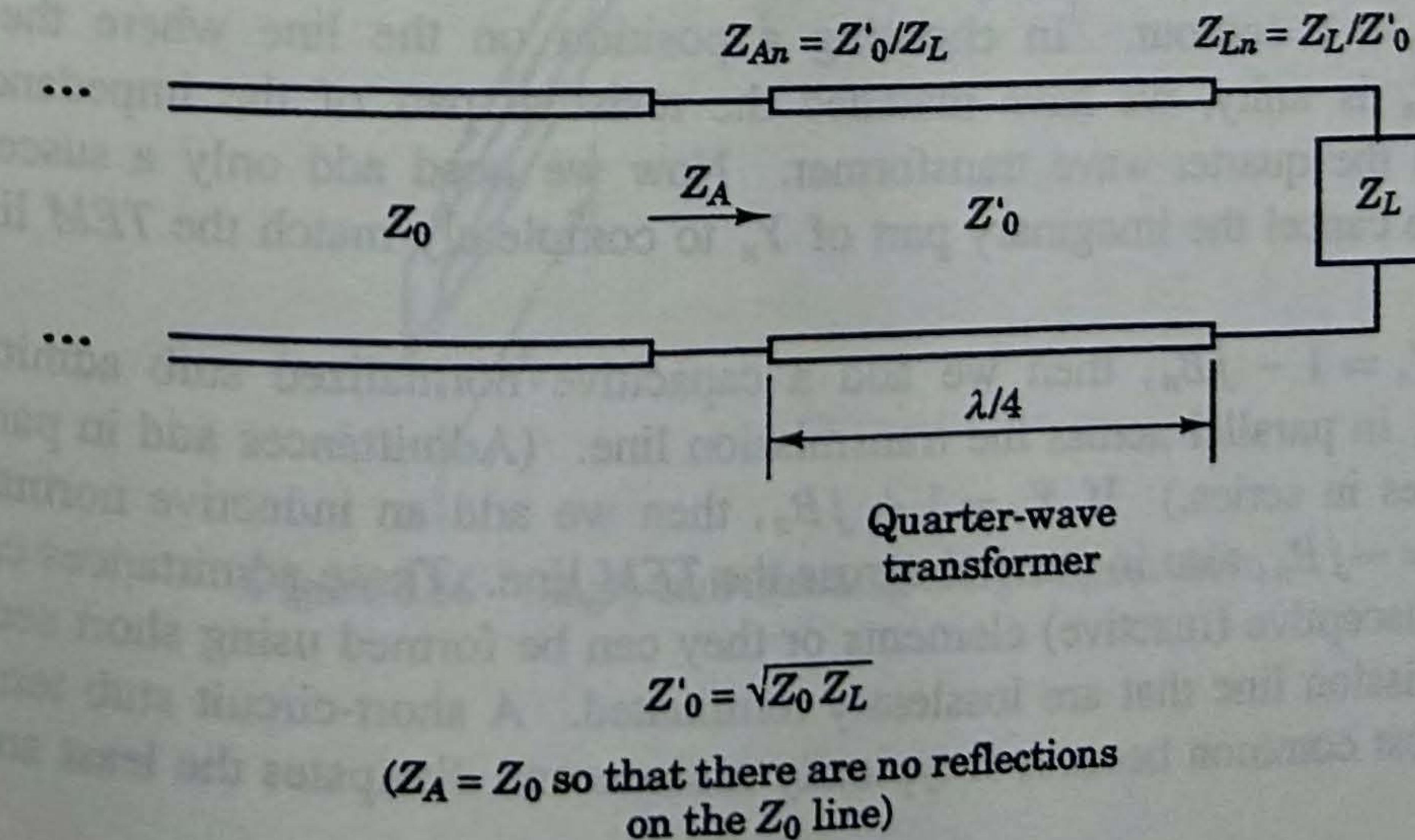


Figure 6.15 Transmission line quarter-wave transformer.

which means that a quarter-wave transformer with characteristic impedance equal to the geometric mean of  $Z_0$  and  $Z_L$  can perfectly match  $Z_0$  to  $Z_L$ . We note that reflections are certainly present on the  $Z'_0$  section of transmission line because the load  $Z_L$  is not matched to  $Z'_0$  nor is  $Z'_0$  matched to  $Z_0$ , but these reflections are confined to the  $Z'_0$  TEM line. If that line is lossless, then all of the power must eventually be dissipated in the load.

One of the principal uses of a Smith chart is in design. For example, it is often desirable to couple power from a source to a load with maximum efficiency, as was illustrated by the quarter-wave transformer when the load is purely resistive. We find this maximum efficiency condition by considering a voltage source  $V_S$  connected to a source impedance  $Z_S$  in series with a load impedance  $Z_L$ . The power dissipated in the load is given by

$$\begin{aligned} P_d &= \frac{1}{2} \operatorname{Re}\{V_L I_L^*\} = \frac{1}{2} |I_L|^2 \operatorname{Re}\{Z_L\} = \frac{1}{2} \left| \frac{V_S}{Z_S + Z_L} \right|^2 \operatorname{Re}\{Z_L\} \\ &= \frac{|V_S|^2}{2} \frac{R_L}{(R_S + R_L)^2 + (X_S + X_L)^2} \end{aligned} \quad (6.3.12)$$

If we now maximize  $P_d$  with respect to  $R_L$  and  $X_L$  by setting  $\partial P_d / \partial R_L = \partial P_d / \partial X_L = 0$ , we find that  $R_L = R_S$  and  $X_L = -X_S$ ; these are the *matching conditions*.

Consider a load of normalized admittance  $Y_{L_n}$  connected to a TEM line. If we move back toward the generator along the line, we trace out a clockwise circle of radius  $|\Gamma_L|$  in the gamma plane, where  $\Gamma_L$  is found from  $Y_{L_n}$ . This circle intersects the contour  $R_n = 1$  at two places, as shown in Figure 6.16, so at two positions within a half wavelength of the load, the admittance is  $Y_n = 1 \pm jB_n$ . The distance between the load and the stub is found by computing the number of wavelengths necessary to rotate the normalized load admittance around to the  $R_n = 1$  contour. In choosing a position on the line where the real part of  $Y_n$  is unity, we have matched the resistive part of the impedance as we did in the quarter-wave transformer. Now we need add only a susceptive element to cancel the imaginary part of  $Y_n$  to completely match the TEM line to the load.

If  $Y_n = 1 - jB_n$ , then we add a capacitive normalized stub admittance  $Y_{sn} = jB_n$  in parallel across the transmission line. (Admittances add in parallel, impedances in series.) If  $Y_n = 1 + jB_n$ , then we add an inductive normalized stub  $Y_{sn} = -jB_n$ , also in parallel across the TEM line. These admittances can be lumped susceptive (reactive) elements or they can be formed using short sections of transmission line that are losslessly terminated. A short-circuit stub termination is most common because it typically radiates and dissipates the least amount

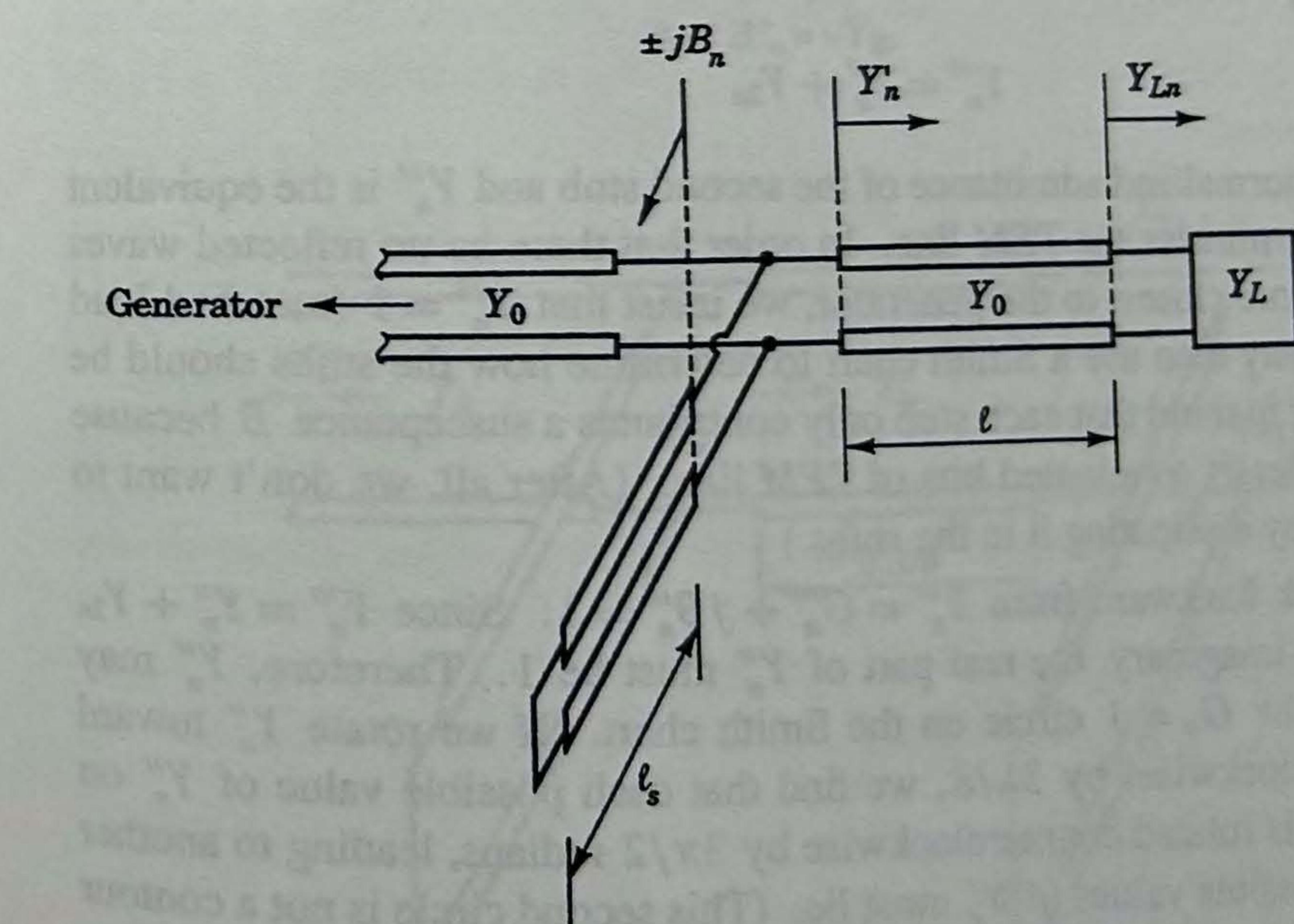
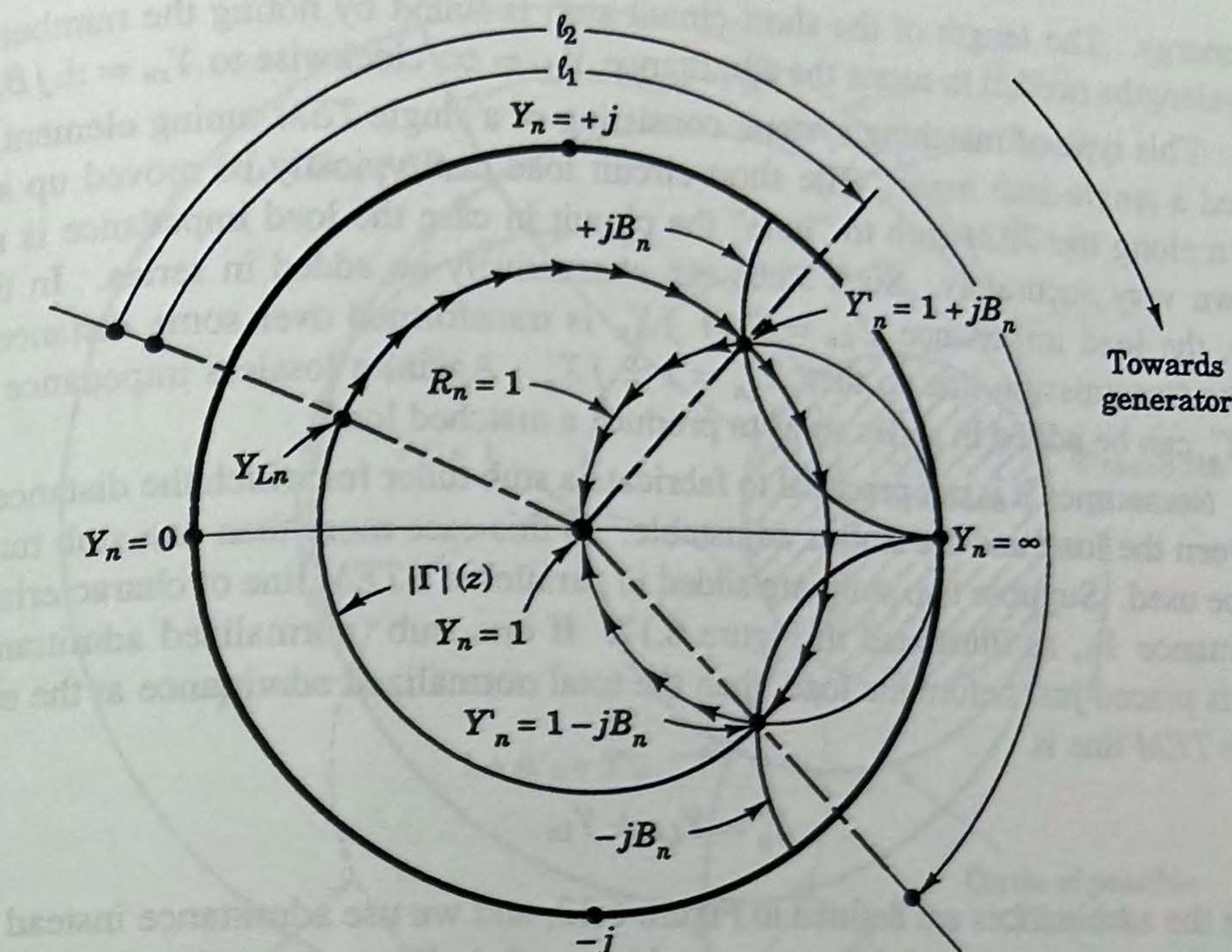


Figure 6.16 Single-stub matching using a Smith chart.